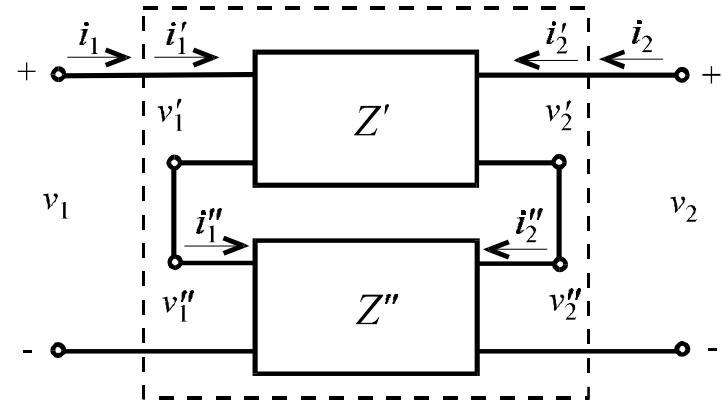


# Interconnecting Networks


- Certain networks are more advantageous to interconnect.

Example: series connection




$$[Z] = [Z'] + [Z'']$$

## • Hybrid representation

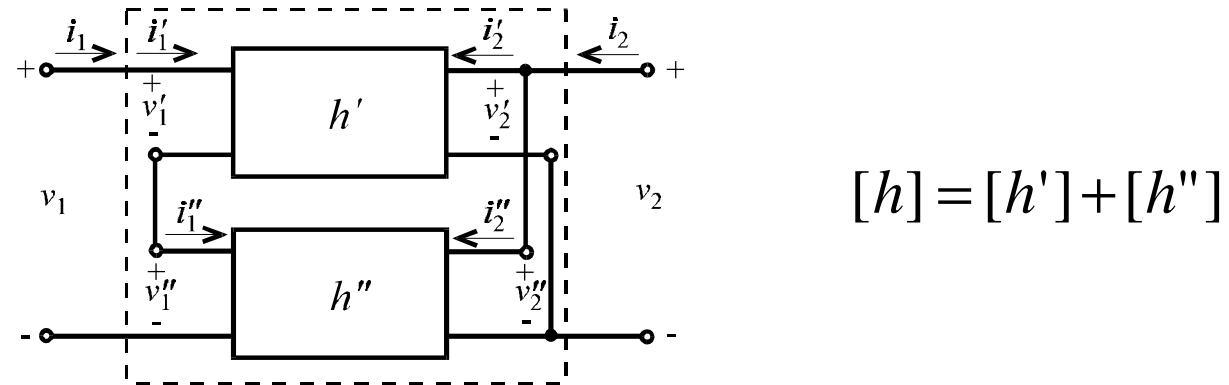


Typical example

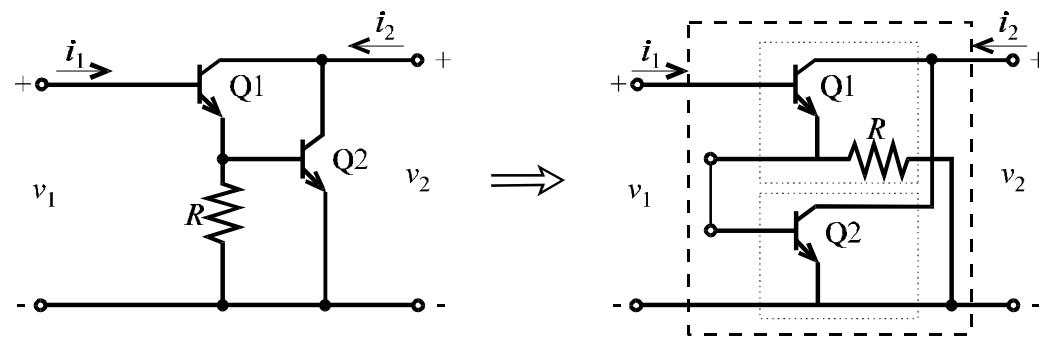


## ABCD parameter representation

- Very useful when cascading networks

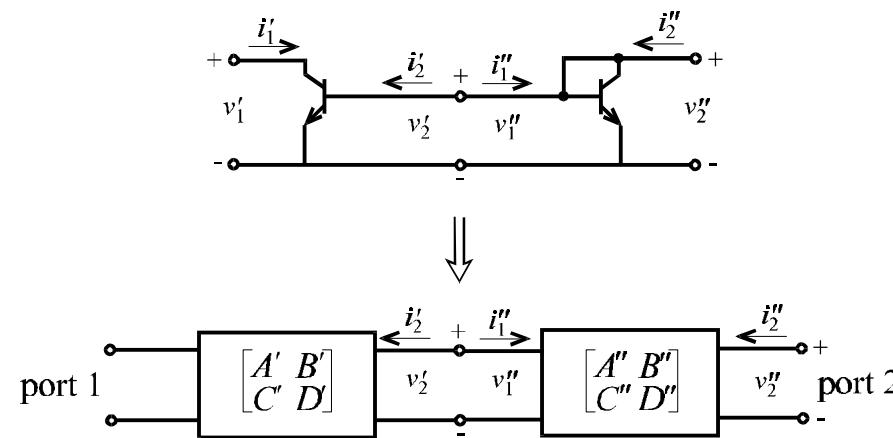

$$\begin{Bmatrix} v_1 \\ i_1 \end{Bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} A'' & B'' \\ C'' & D'' \end{bmatrix} \begin{Bmatrix} v_1'' \\ -i_2'' \end{Bmatrix}$$

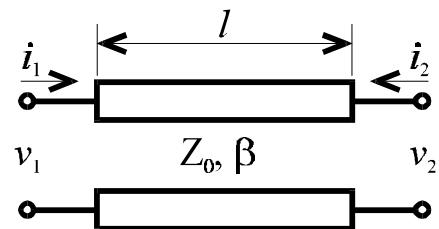ABCD network is very useful for transmission line representations



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos(\mathbf{bl}) & jZ_0 \sin(\mathbf{bl}) \\ j \frac{\sin(\mathbf{bl})}{Z_0} & \cos(\mathbf{bl}) \end{bmatrix}$$

Example:

